

Ch21 Concept





Tuesday, 27 October 2020 20:48

Circuit

V = Voltage [$V_{(Volt)}$] = Voltmeter ($\infty \Omega$ & // Resistor)
I = Current [$A_{(Ampere)}$] = Ammeter (0Ω & in series)
R = Resistance [$\Omega_{(ohm)}$] = $V = IR$
P = Power [$W_{(Watt)}$] = $P = VI \parallel = \frac{E}{t}$
E = Energy [$J_{(Joule)}$] = $E = Pt$
Q = Charges (Total) [$C_{(Coulomb)}$]

Measurement

Hardware

potentiometer  [Functional Same!]
Reostat  (Rotary)
Thermistor  [Semi conductor]
Diode  [One way for particle]

Voltage & Current

Definition

$$I = \frac{Q}{t} = \frac{Nq}{t}$$

(N = Total n Particle
q = Charges of each part.)

$$[A] = [C \cdot s^{-1}]$$

$$V = \frac{E}{Q}$$


$$[V] = [J \cdot C^{-1}]$$


Voltage

$\mathcal{E} = \text{e.m.f} \rightarrow \text{|||}$
 $V_{p.d} = \text{potential difference} \rightarrow \text{---}$

Ideal case

$\mathcal{E} = \text{p.d. in EACH closed circuit}$


In Series 
 $\mathcal{E} = V_1 + V_2$

In parallel 
 $\mathcal{E} = V_1 + V_2$
 $\mathcal{E} = V_3$

$$V = IR \text{ (ohm's law)}$$

$$[V] = [A \Omega]$$

$$\parallel [A \Omega] = [VA^{-1}]$$

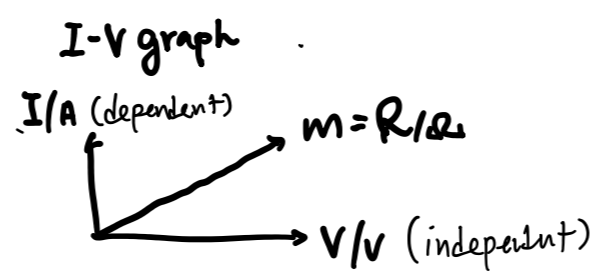

I-V graph
 $m = \text{st. line} \Rightarrow \text{const. } R \Rightarrow \text{Ohmic}$

$$m \propto \frac{1}{R}$$


$$V = I \cdot R$$

Resistivity = ρ [Ωm]

$$\rho = \frac{R \cdot A_{(cross \ section \ area)}}{l_{(length)}}$$

$$[\Omega m] = [\Omega \frac{m^2}{m}]$$

Non-Ohmic

- semi-conductor
 $I \propto \frac{1}{R}$ 

Resistors

In Series

$$\sum V = V_1 + V_2 + \dots + V_n$$

$$\therefore I \sum R = [(R_1 + R_2 + \dots + R_n)]$$

* Const. I in same branch

$$\therefore \sum R = R_1 + R_2 + \dots + R_n$$

Parallel

$$\frac{1}{\sum R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

* Parallel w/ same p.d.

$$\sum R = \frac{R}{n}$$

or $\sum R^{-1} = R_1^{-1} + R_2^{-1} + \dots + R_n^{-1}$

Share of Voltage ^{* Ch22}



$$\therefore V_1 + V_2 = \sum V$$

$$R_1 + R_2 = \sum R$$

$$I = \frac{\sum V}{\sum R}$$

For each p.d V

$$V_i = IR_i$$

$$V_i = \frac{\sum V}{\sum R} \cdot R_i$$

$$V_i = \frac{R_i}{R_1 + R_2} \cdot \sum V$$

$$\rightarrow V_n = \frac{R_n}{\sum R} \cdot \sum V$$

Power

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$P = \mathcal{E}I$$

sub # Ideal case
 Light Brightness (which is Pwr)

Series (I const.)

$$P = I^2 R$$

$$P \propto R$$

Parallel (V const.)

$$P = \frac{V^2}{R}$$

$$P \propto \frac{1}{R}$$

$$1 \text{ kWh} = \frac{1000 \text{ W}}{3600 \text{ s}} \Rightarrow 3.6 \text{ MJ}$$

* Ch22


$$3.6 \times 6 \text{ J}$$

Nothing is Ideal

IRL

$$\mathcal{E} \neq V_{p.d}$$
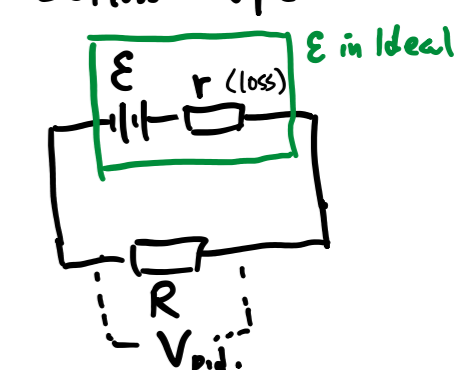
$$\mathcal{E} \text{ w/ loss} = V_{p.d}$$





$$\mathcal{E} = I(R+r) = V + Ir$$

$$V = \mathcal{E} - Ir$$

$$p.d = \text{emf} - \text{emf loss}$$

(A)/(V) in non-Ideal circuit

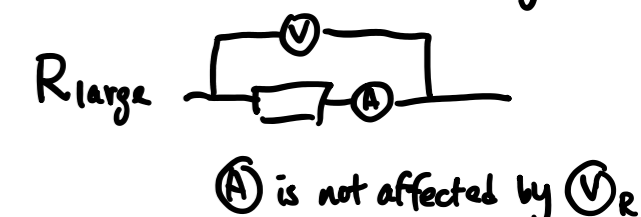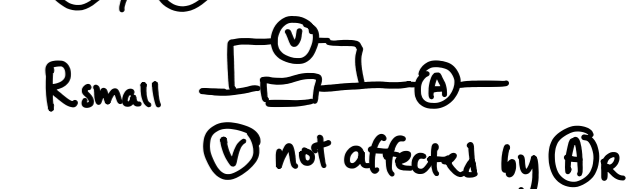

Checked
 Yohus ©
 27 Oct, 2020